

Bridge Circuits

Objectives:

State the purpose of a bridge circuit.

Identify a bridge circuit.

Solve for voltage outputs.

Solve for unknown resistance.


Measure voltages in a bridge circuit.

Measure resistance in a bridge circuit.

Bridge Circuits


Compare know values to unknown values.

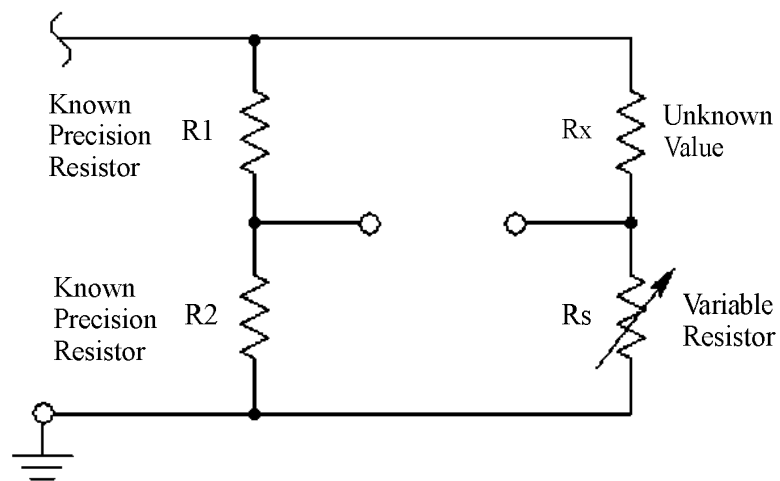A bridge circuit is two voltage dividers wired in parallel.




The voltage divider of R_1 and R_2 are a reference.

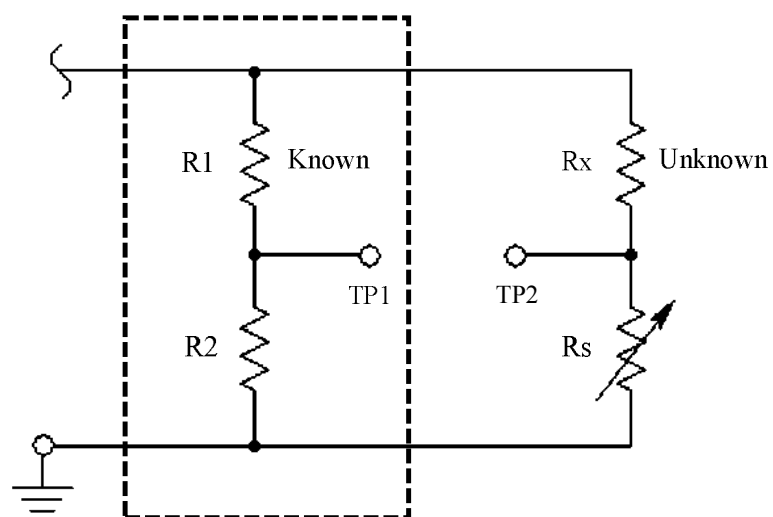The voltage at TP1 will always be the same for that voltage divider.



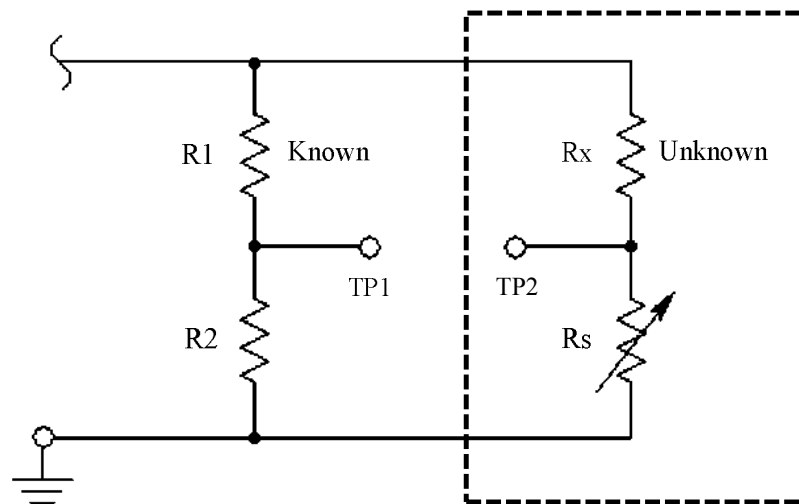The voltage divider of R_x and R_s are unknown.
 R_x will change due to outside forces.
This will cause the voltage at TP2 to change.





The voltage between TP1 and TP2 are compared for differences.

If no difference exists, the output will be 0V. This is known as balanced.

If TP2 is more than TP1, E_{OUT} will be positive.

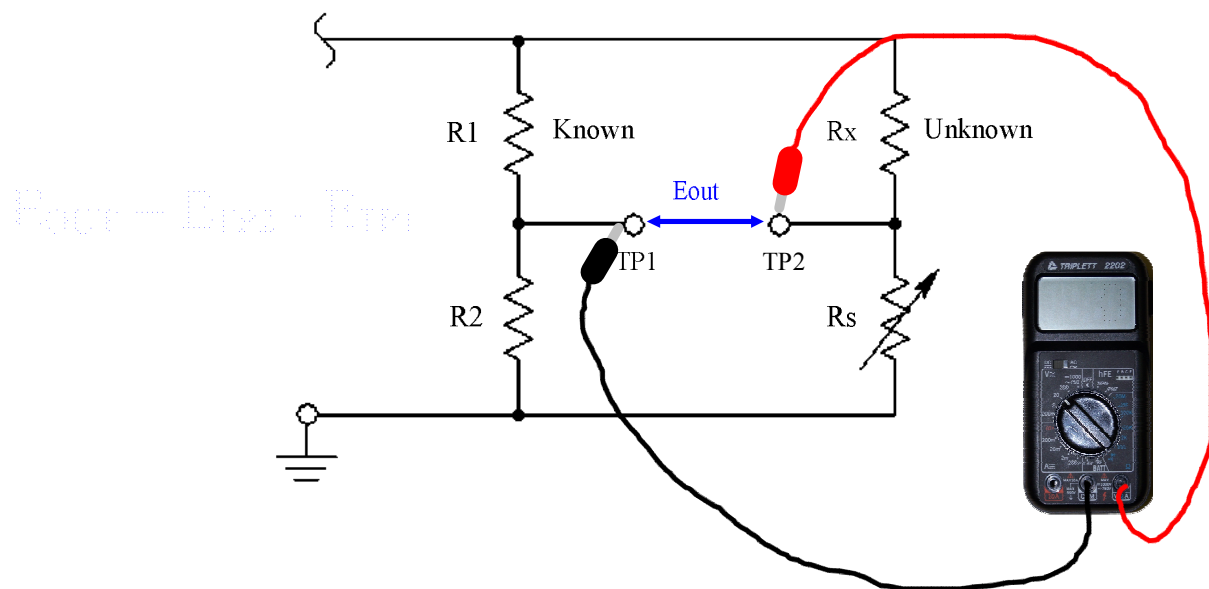If TP2 is less than TP1, E_{OUT} will be negative.




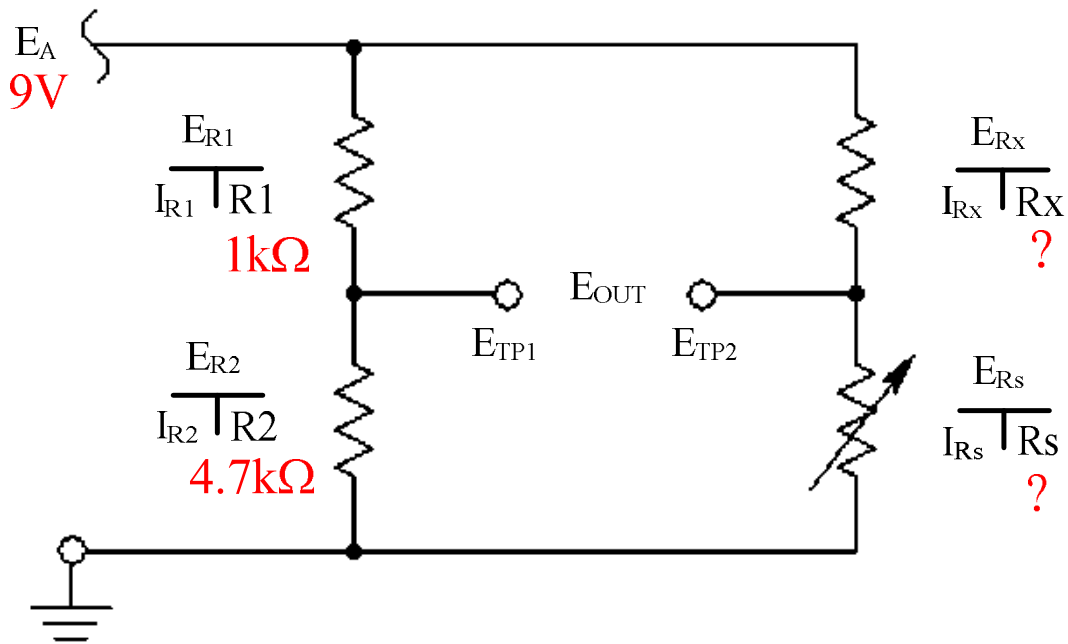


$E_{TP1} =$ _____

$E_{TP2} =$ _____

$E_{OUT} =$ _____

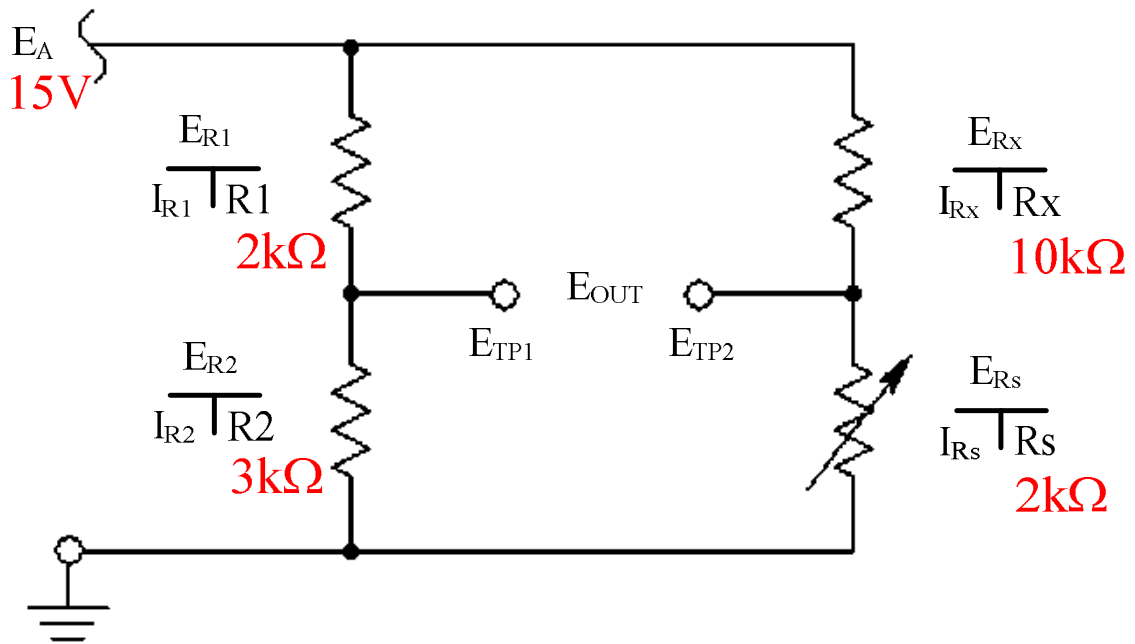

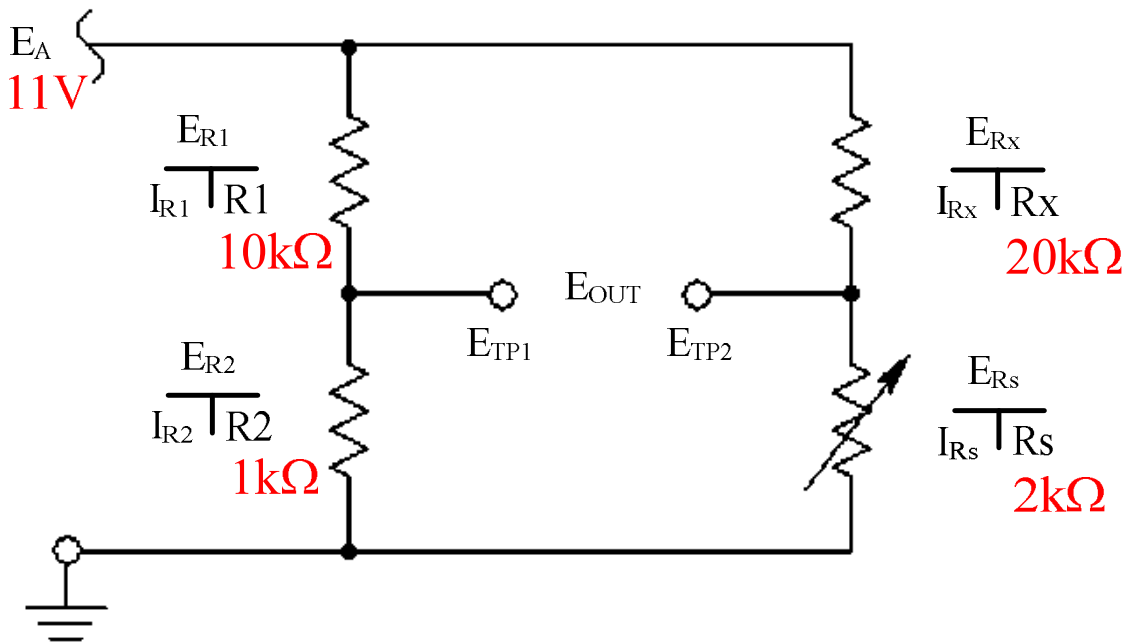
$E_{TP1} =$ _____
 $E_{TP2} =$ _____
 $E_{OUT} =$ _____



$E_{TP1} =$ _____

$E_{TP2} =$ _____

$E_{OUT} =$ _____

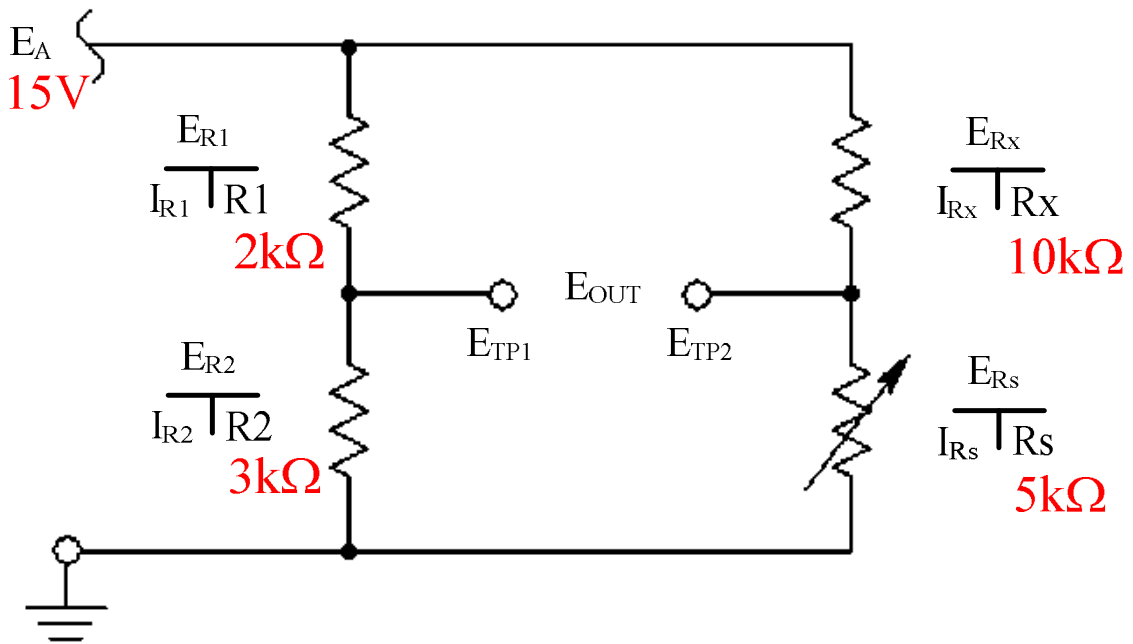

$E_{TP1} =$ _____
 $E_{TP2} =$ _____
 $E_{OUT} =$ _____