

Series Circuits

Objectives:

- Identify a series circuit.
- Calculate total resistance in a series circuit.
- Calculate current in a series circuit.
- Calculate voltage drops across resistance.
- Measure current values in a series circuit.
- Measure voltage drops in a series circuit.

Series Circuit: Circuit with only one path for current to flow.

Total Resistance: Sum of all resistors.


$$R_T = R_1 + R_2 + R_3 + \dots$$

Total Current: Same throughout the circuit path.

$$I_T = I_{R1} = I_{R2} = I_{R3} = \dots$$

Total Voltage: Sum of all voltage drops.

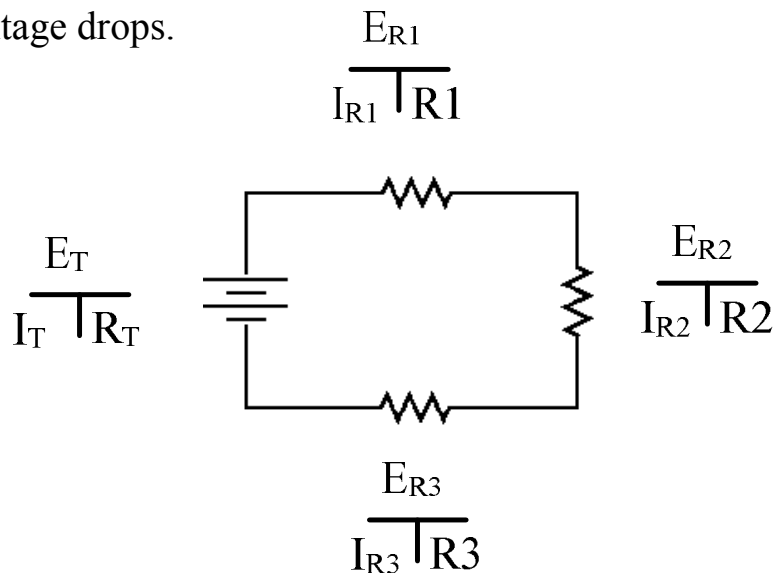
$$V_T = V_{R1} + V_{R2} + V_{R3} + \dots$$



$$R_T = R_1 + R_2 + R_3 + \dots$$

$$I_T = I_{R1} = I_{R2} = I_{R3} = \dots$$
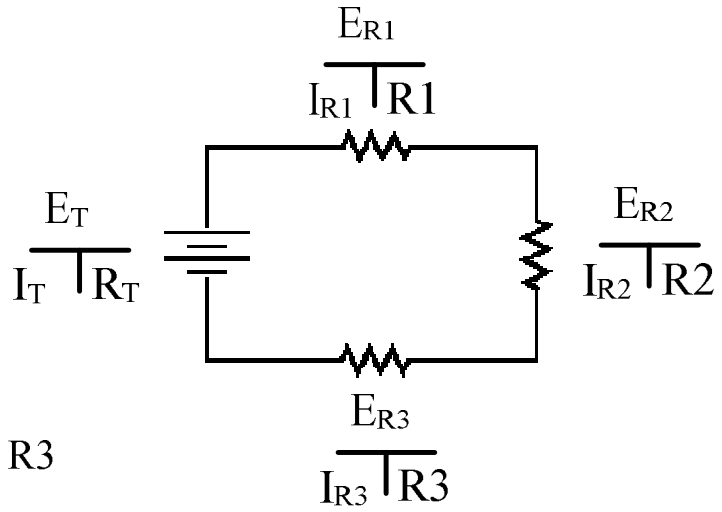
$$V_T = V_{R1} + V_{R2} + V_{R3} + \dots$$



Step 1. Find $R_T = R_1 + R_2 + R_3$

Step 2. Find $I_T = \frac{E_T}{R_T}$

Step 3. Find Voltage Drops

$$E_{R1} = I_{R1} \times R_1$$

$$E_{R2} = I_{R2} \times R_2$$


$$E_{R3} = I_{R3} \times R_3$$

	V	I	R
Short	0V	Max	0Ω
Open	Max	0A	∞

$$R_T = R_1 + R_2 + R_3 + \dots$$

$$I_T = I_{R1} = I_{R2} = I_{R3} = \dots$$
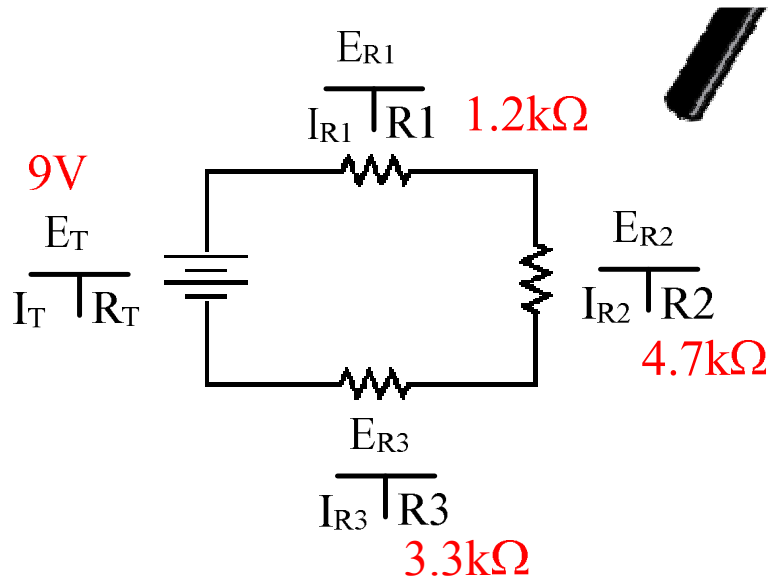
$$V_T = V_{R1} + V_{R2} + V_{R3} + \dots$$



Reveal

Step 1. Find $R_T =$

Reveal

Step 2. Find $I_T =$

Reveal

Step 3. Find Voltage Drops

$$E_{R1} =$$

$$E_{R2} =$$


$$E_{R3} =$$

	V	I	R
Short	0V	Max	0Ω
Open	Max	0A	∞

$$R_T = R_1 + R_2 + R_3 + \dots$$

$$I_T = I_{R1} = I_{R2} = I_{R3} = \dots$$
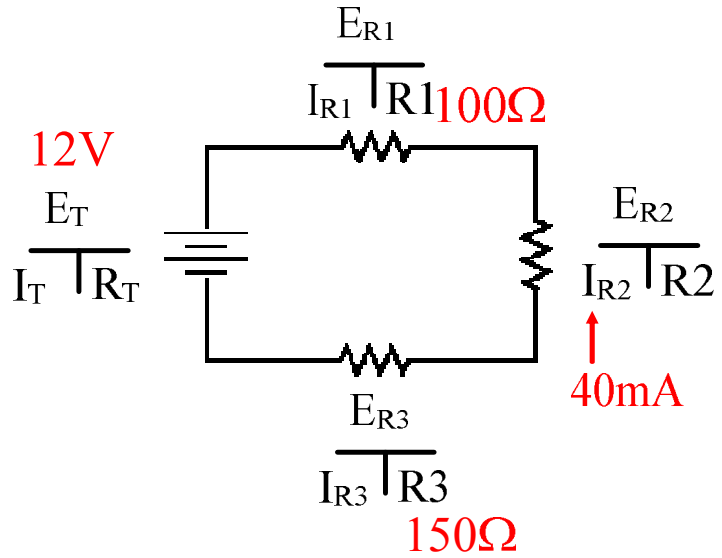
$$V_T = V_{R1} + V_{R2} + V_{R3} + \dots$$



Reveal

Step 1. Find $R_T =$

Reveal

Step 2. Find $I_T =$

Reveal

Step 3. Find Voltage Drops

$$E_{R1} =$$

$$E_{R2} =$$

$$E_{R3} =$$

	V	I	R
Short	0V	Max	0Ω
Open	Max	0A	∞